



Two-port network

In electronics, a **two-port network** (a kind of **four-terminal network** or **quadripole**) is an electrical network (i.e. a circuit) or device with two *pairs* of terminals to connect to external circuits. Two terminals constitute a port if the currents applied to them satisfy the essential requirement known as the port condition: the current entering one terminal must equal the current emerging from the other terminal on the same port.^{[1][2]} The ports constitute interfaces where the network connects to other networks, the points where signals are applied or outputs are taken. In a two-port network, often port 1 is considered the input port and port 2 is considered the output port.

It is commonly used in mathematical circuit analysis.

Application

The two-port network model is used in mathematical circuit analysis techniques to isolate portions of larger circuits. A two-port network is regarded as a "black box" with its properties specified by a matrix of numbers. This allows the response of the network to signals applied to the ports to be calculated easily, without solving for all the internal voltages and currents in the network. It also allows similar circuits or devices to be compared easily. For example, transistors are often regarded as two-ports, characterized by their *h*-parameters (see below) which are listed by the manufacturer. Any linear circuit with four terminals can be regarded as a two-port network provided that it does not contain an independent source and satisfies the port conditions.

Examples of circuits analyzed as two-ports are filters, matching networks, transmission lines, transformers, and small-signal models for transistors (such as the hybrid-pi model). The analysis of passive two-port networks is an outgrowth of reciprocity theorems first derived by Lorentz.^[3]

In two-port mathematical models, the network is described by a 2 by 2 square matrix of complex numbers. The common models that are used are referred to as *z*-parameters, *y*-parameters, *h*-parameters, *g*-parameters, and *ABCD*-parameters, each described individually below. These are all limited to linear networks since an underlying assumption of their derivation is that any given circuit condition is a linear superposition of various short-circuit and open circuit conditions. They are usually expressed in matrix notation, and they establish relations between the variables

V_1 , voltage across port 1
 I_1 , current into port 1
 V_2 , voltage across port 2
 I_2 , current into port 2

which are shown in figure 1. The difference between the various models lies in which of these variables are regarded as the independent variables. These current and voltage variables are most useful at low-to-moderate frequencies. At high frequencies (e.g., microwave frequencies), the use of power and energy variables is more appropriate, and the two-port current-voltage approach is replaced by an approach based upon scattering parameters.

General properties

There are certain properties of two-ports that frequently occur in practical networks and can be used to greatly simplify the analysis. These include:

Reciprocal networks

A network is said to be reciprocal if the voltage appearing at port 2 due to a current applied at port 1 is the same as the voltage appearing at port 1 when the same current is applied to port 2. Exchanging voltage and current results in an equivalent definition of reciprocity. A network that consists entirely of linear passive components (that is, resistors, capacitors and inductors) is usually reciprocal, a notable exception being passive circulators and isolators that contain magnetized materials. In general, it *will not* be reciprocal if it contains active components such as generators or transistors.^[4]

Symmetrical networks

A network is symmetrical if its input impedance is equal to its output impedance. Most often, but not necessarily, symmetrical networks are also physically symmetrical. Sometimes also antimetrical networks are of interest. These are networks where the input and output impedances are the duals of each other.^[5]

Lossless network

A lossless network is one which contains no resistors or other dissipative elements.^[6]

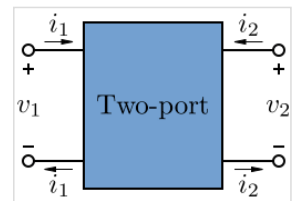


Figure 1: Example two-port network with symbol definitions. Notice the **port condition** is satisfied: the same current flows into each port as leaves that port.

Impedance parameters (z-parameters)

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

where

$$\begin{aligned} z_{11} &\stackrel{\text{def}}{=} \frac{V_1}{I_1} \bigg|_{I_2=0} & z_{12} &\stackrel{\text{def}}{=} \frac{V_1}{I_2} \bigg|_{I_1=0} \\ z_{21} &\stackrel{\text{def}}{=} \frac{V_2}{I_1} \bigg|_{I_2=0} & z_{22} &\stackrel{\text{def}}{=} \frac{V_2}{I_2} \bigg|_{I_1=0} \end{aligned}$$

All the z-parameters have dimensions of ohms.

For reciprocal networks $z_{12} = z_{21}$. For symmetrical networks $z_{11} = z_{22}$. For reciprocal lossless networks all the z_{mn} are purely imaginary.^[7]

Example: bipolar current mirror with emitter degeneration

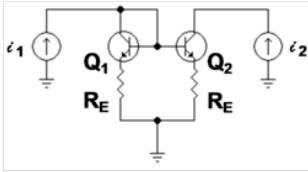


Figure 3: Bipolar current mirror: i_1 is the reference current and i_2 is the output current; lower case symbols indicate these are total currents that include the DC components

Figure 3 shows a bipolar current mirror with emitter resistors to increase its output resistance.^[nb 1] Transistor Q_1 is *diode connected*, which is to say its collector-base voltage is zero. Figure 4 shows the small-signal circuit equivalent to Figure 3. Transistor Q_1 is represented by its emitter resistance r_E :

$$r_E \approx \frac{\text{thermal voltage, } V_T}{\text{emitter current, } I_E},$$

a simplification made possible because the dependent current source in the hybrid- π model for

Q_1 draws the same current as a resistor $1/g_m$ connected across r_π . The second transistor Q_2 is represented by its hybrid- π model. Table 1 below shows the z-parameter expressions that make the z-equivalent circuit of Figure 2 electrically equivalent to the small-signal circuit of Figure 4.

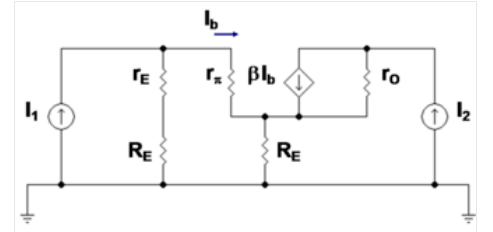


Figure 4: Small-signal bipolar current mirror: I_1 is the amplitude of the small-signal reference current and I_2 is the amplitude of the small-signal output current

Table 1

	Expression	Approximation
$R_{21} = \frac{V_2}{I_1} \bigg _{I_2=0}$	$-(\beta r_O - R_E) \frac{r_E + R_E}{r_\pi + r_E + 2R_E}$	$-\beta r_O \frac{r_E + R_E}{r_\pi + 2R_E}$
$R_{11} = \frac{V_1}{I_1} \bigg _{I_2=0}$	$(r_E + R_E) \parallel (r_\pi + R_E)$ ^[nb 2]	
$R_{22} = \frac{V_2}{I_2} \bigg _{I_1=0}$	$\left(1 + \beta \frac{R_E}{r_\pi + r_E + 2R_E}\right) r_O + \frac{r_\pi + r_E + R_E}{r_\pi + r_E + 2R_E} R_E$	$\left(1 + \beta \frac{R_E}{r_\pi + 2R_E}\right) r_O$
$R_{12} = \frac{V_1}{I_2} \bigg _{I_1=0}$	$R_E \frac{r_E + R_E}{r_\pi + r_E + 2R_E}$	$R_E \frac{r_E + R_E}{r_\pi + 2R_E}$

The negative feedback introduced by resistors R_E can be seen in these parameters. For example, when used as an active load in a differential amplifier, $I_1 \approx -I_2$, making the output impedance of the mirror approximately

$$R_{22} - R_{21} \approx \frac{2\beta r_O R_E}{r_\pi + 2R_E}$$

compared to only r_O without feedback (that is with $R_E = 0 \Omega$). At the same time, the impedance on the reference side of the mirror is approximately

$$R_{11} - R_{12} \approx \frac{r_\pi}{r_\pi + 2R_E} (r_E + R_E),$$

only a moderate value, but still larger than r_E with no feedback. In the differential amplifier application, a large output resistance increases the difference-mode gain, a good thing, and a small mirror input resistance is desirable to avoid Miller effect.

Admittance parameters (y-parameters)

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

where

$$\begin{aligned} y_{11} &\stackrel{\text{def}}{=} \left. \frac{I_1}{V_1} \right|_{V_2=0} & y_{12} &\stackrel{\text{def}}{=} \left. \frac{I_1}{V_2} \right|_{V_1=0} \\ y_{21} &\stackrel{\text{def}}{=} \left. \frac{I_2}{V_1} \right|_{V_2=0} & y_{22} &\stackrel{\text{def}}{=} \left. \frac{I_2}{V_2} \right|_{V_1=0} \end{aligned}$$

All the Y-parameters have dimensions of siemens.

For reciprocal networks $y_{12} = y_{21}$. For symmetrical networks $y_{11} = y_{22}$. For reciprocal lossless networks all the y_{mn} are purely imaginary.^[7]

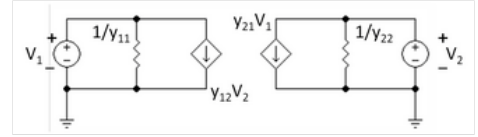


Figure 5: Y-equivalent two port showing independent variables V_1 and V_2 . Although resistors are shown, general admittances can be used instead.

Hybrid parameters (h-parameters)

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

where

$$\begin{aligned} h_{11} &\stackrel{\text{def}}{=} \left. \frac{V_1}{I_1} \right|_{V_2=0} & h_{12} &\stackrel{\text{def}}{=} \left. \frac{V_1}{V_2} \right|_{I_1=0} \\ h_{21} &\stackrel{\text{def}}{=} \left. \frac{I_2}{I_1} \right|_{V_2=0} & h_{22} &\stackrel{\text{def}}{=} \left. \frac{I_2}{V_2} \right|_{I_1=0} \end{aligned}$$

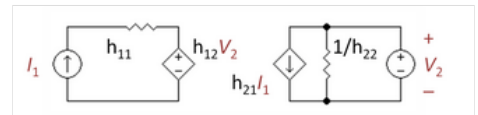


Figure 6: H-equivalent two-port showing independent variables I_1 and V_2 ; h_{22} is reciprocated to make a resistor

This circuit is often selected when a current amplifier is desired at the output. The resistors shown in the diagram can be general impedances instead.

Off-diagonal h -parameters are dimensionless, while diagonal members have dimensions the reciprocal of one another.

For reciprocal networks $h_{12} = -h_{21}$. For symmetrical networks $h_{11}h_{22} - h_{12}h_{21} = 1$. For reciprocal lossless networks h_{12} and h_{21} are real, while h_{11} and h_{22} are purely imaginary.

Example: common-base amplifier

Note: Tabulated formulas in Table 2 make the h -equivalent circuit of the transistor from Figure 6 agree with its small-signal low-frequency hybrid-pi model in Figure 7. Notation: r_π is base resistance of transistor, r_O is output resistance, and g_m is mutual transconductance. The negative sign for h_{21} reflects the convention that I_1 , I_2 are positive when directed *into* the two-port. A non-zero value for h_{12} means the output voltage affects the input voltage, that is, this amplifier is **bilateral**. If $h_{12} = 0$, the amplifier is **unilateral**.

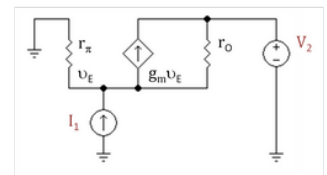


Figure 7: Common-base amplifier with AC current source I_1 as signal input and unspecified load supporting voltage V_2 and a dependent current I_2 .

Table 2

	Expression	Approximation
$h_{21} = \frac{I_2}{I_1} \Big _{V_2=0}$	$-\frac{\frac{\beta}{\beta+1}r_O + r_\pi}{r_O + r_\pi}$	$-\frac{\beta}{\beta+1}$
$h_{11} = \frac{V_1}{I_1} \Big _{V_2=0}$	$r_\pi \parallel r_O$	r_π
$h_{22} = \frac{I_2}{V_2} \Big _{I_1=0}$	$\frac{1}{(\beta+1)(r_O + r_\pi)}$	$\frac{1}{(\beta+1)r_O}$
$h_{12} = \frac{V_1}{V_2} \Big _{I_1=0}$	$\frac{r_\pi}{r_O + r_\pi}$	$\frac{r_\pi}{r_O} \ll 1$

History

The h -parameters were initially called *series-parallel parameters*. The term *hybrid* to describe these parameters was coined by D. A. Alsberg in 1953 in "Transistor metrology".^[8] In 1954 a joint committee of the IRE and the AIEE adopted the term h -parameters and recommended that these become the standard method of testing and characterising transistors because they were "peculiarly adaptable to the physical characteristics of transistors".^[9] In 1956, the recommendation became an issued standard; 56 IRE 28.S2. Following the merge of these two organisations as the IEEE, the standard became Std 218-1956 and was reaffirmed in 1980, but has now been withdrawn.^[10]

Inverse hybrid parameters (g-parameters)

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

where

$$\begin{aligned} g_{11} &\stackrel{\text{def}}{=} \frac{I_1}{V_1} \Big|_{I_2=0} & g_{12} &\stackrel{\text{def}}{=} \frac{I_1}{I_2} \Big|_{V_1=0} \\ g_{21} &\stackrel{\text{def}}{=} \frac{V_2}{V_1} \Big|_{I_2=0} & g_{22} &\stackrel{\text{def}}{=} \frac{V_2}{I_2} \Big|_{V_1=0} \end{aligned}$$

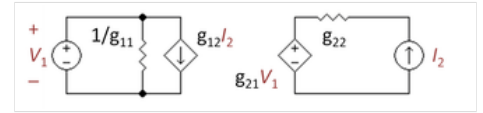


Figure 8: G-equivalent two-port showing independent variables V_1 and I_2 ; g_{11} is reciprocated to make a resistor

Often this circuit is selected when a voltage amplifier is wanted at the output. Off-diagonal g -parameters are dimensionless, while diagonal members have dimensions the reciprocal of one another. The resistors shown in the diagram can be general impedances instead.

Example: common-base amplifier

Note: Tabulated formulas in Table 3 make the g -equivalent circuit of the transistor from Figure 8 agree with its small-signal low-frequency hybrid-pi model in Figure 9. Notation: r_π is base resistance of transistor, r_O is output resistance, and g_m is mutual transconductance. The negative sign for g_{12} reflects the convention that I_1 , I_2 are positive when directed *into* the two-port. A non-zero value for g_{12} means the output current affects the input current, that is, this amplifier is **bilateral**. If $g_{12} = 0$, the amplifier is **unilateral**.

Table 3

	Expression	Approximation
$g_{21} = \frac{V_2}{V_1} \Big _{I_2=0}$	$\frac{r_O}{r_\pi} + g_m r_O + 1$	$g_m r_O$
$g_{11} = \frac{I_1}{V_1} \Big _{I_2=0}$	$\frac{1}{r_\pi}$	$\frac{1}{r_\pi}$
$g_{22} = \frac{V_2}{I_2} \Big _{V_1=0}$	r_O	r_O
$g_{12} = \frac{I_1}{I_2} \Big _{V_1=0}$	$-\frac{\beta+1}{\beta}$	-1

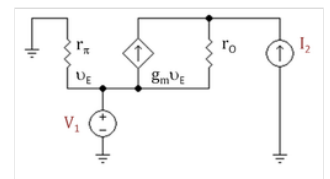


Figure 9: Common-base amplifier with AC voltage source V_1 as signal input and unspecified load delivering current I_2 at a dependent voltage V_2 .

ABCD-parameters

The *ABCD*-parameters are known variously as chain, cascade, or transmission parameters. There are a number of definitions given for *ABCD* parameters, the most common is,^{[11][12]}

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Note: Some authors chose to reverse the indicated direction of I_2 and suppress the negative sign on I_2 .

where

$$\begin{aligned} A &\stackrel{\text{def}}{=} \left. \frac{V_1}{V_2} \right|_{I_2=0} & B &\stackrel{\text{def}}{=} - \left. \frac{V_1}{I_2} \right|_{V_2=0} \\ C &\stackrel{\text{def}}{=} \left. \frac{I_1}{V_2} \right|_{I_2=0} & D &\stackrel{\text{def}}{=} - \left. \frac{I_1}{I_2} \right|_{V_2=0} \end{aligned}$$

For reciprocal networks $AD - BC = 1$. For symmetrical networks $A = D$. For networks which are reciprocal and lossless, A and D are purely real while B and C are purely imaginary.^[6]

This representation is preferred because when the parameters are used to represent a cascade of two-ports, the matrices are written in the same order that a network diagram would be drawn, that is, left to right. However, a variant definition is also in use,^[13]

$$\begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}$$

where

$$\begin{aligned} A' &\stackrel{\text{def}}{=} \left. \frac{V_2}{V_1} \right|_{I_1=0} & B' &\stackrel{\text{def}}{=} \left. \frac{V_2}{I_1} \right|_{V_1=0} \\ C' &\stackrel{\text{def}}{=} - \left. \frac{I_2}{V_1} \right|_{I_1=0} & D' &\stackrel{\text{def}}{=} - \left. \frac{I_2}{I_1} \right|_{V_1=0} \end{aligned}$$

The negative sign of $-I_2$ arises to make the output current of one cascaded stage (as it appears in the matrix) equal to the input current of the next. Without the minus sign the two currents would have opposite senses because the positive direction of current, by convention, is taken as the current entering the port. Consequently, the input voltage/current matrix vector can be directly replaced with the matrix equation of the preceding cascaded stage to form a combined $A'B'C'D'$ matrix.

The terminology of representing the *ABCD* parameters as a matrix of elements designated a_{11} etc. as adopted by some authors^[14] and the inverse $A'B'C'D'$ parameters as a matrix of elements designated b_{11} etc. is used here for both brevity and to avoid confusion with circuit elements.

$$\begin{aligned} [\mathbf{a}] &= \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \\ [\mathbf{b}] &= \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \end{aligned}$$

Table of transmission parameters

The table below lists *ABCD* and inverse *ABCD* parameters for some simple network elements.

Element	[a] matrix	[b] matrix	Remarks
Series impedance	$\begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$	$\begin{bmatrix} 1 & -Z \\ 0 & 1 \end{bmatrix}$	Z , impedance
Shunt admittance	$\begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$	$\begin{bmatrix} 1 & 0 \\ -Y & 1 \end{bmatrix}$	Y , admittance
Series inductor	$\begin{bmatrix} 1 & sL \\ 0 & 1 \end{bmatrix}$	$\begin{bmatrix} 1 & -sL \\ 0 & 1 \end{bmatrix}$	L , inductance s , complex angular frequency
Shunt inductor	$\begin{bmatrix} 1 & 0 \\ \frac{1}{sL} & 1 \end{bmatrix}$	$\begin{bmatrix} 1 & 0 \\ -\frac{1}{sL} & 1 \end{bmatrix}$	L , inductance s , complex angular frequency
Series capacitor	$\begin{bmatrix} 1 & \frac{1}{sC} \\ 0 & 1 \end{bmatrix}$	$\begin{bmatrix} 1 & -\frac{1}{sC} \\ 0 & 1 \end{bmatrix}$	C , capacitance s , complex angular frequency
Shunt capacitor	$\begin{bmatrix} 1 & 0 \\ sC & 1 \end{bmatrix}$	$\begin{bmatrix} 1 & 0 \\ -sC & 1 \end{bmatrix}$	C , capacitance s , complex angular frequency
Transmission line	$\begin{bmatrix} \cosh(\gamma l) & Z_0 \sinh(\gamma l) \\ \frac{1}{Z_0} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix}$	$\begin{bmatrix} \cosh(\gamma l) & -Z_0 \sinh(\gamma l) \\ -\frac{1}{Z_0} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix}$ ^[15]	Z_0 , characteristic impedance γ , propagation constant ($\gamma = \alpha + i\beta$) l , length of transmission line (m)
Impedance Matching Network $\{Z_S \xrightarrow{\varphi} Z_L\}$ ^[16]	$\frac{1}{\sqrt{R_S R_L}} \begin{bmatrix} \Re(\tilde{Z}_S e^{j\varphi}) & j\Im(\tilde{Z}_S \tilde{Z}_L e^{j\varphi}) \\ j\Im(e^{j\varphi}) & \Re(\tilde{Z}_L e^{j\varphi}) \end{bmatrix}$	$\frac{1}{\sqrt{R_S R_L}} \begin{bmatrix} \Re(\tilde{Z}_L e^{j\varphi}) & -j\Im(\tilde{Z}_S \tilde{Z}_L e^{j\varphi}) \\ -j\Im(e^{j\varphi}) & \Re(\tilde{Z}_S e^{j\varphi}) \end{bmatrix}$	$Z_S = R_S + jX_S$, Source Impedance $Z_L = R_L + jX_L$, Load Impedance φ , Phase Shift $\Re(Z)$, real part of Z $\Im(Z)$, imaginary part of Z

Scattering parameters (S-parameters)

The previous parameters are all defined in terms of voltages and currents at ports. S -parameters are different, and are defined in terms of incident and reflected waves at ports. S -parameters are used primarily at UHF and microwave frequencies where it becomes difficult to measure voltages and currents directly. On the other hand, incident and reflected power are easy to measure using directional couplers. The definition is, ^[17]

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

where the a_k are the incident waves and the b_k are the reflected waves at port k . It is conventional to define the a_k and b_k in terms of the square root of power. Consequently, there is a relationship with the wave voltages (see main article for details). ^[18]

For reciprocal networks $S_{12} = S_{21}$. For symmetrical networks $S_{11} = S_{22}$. For antimetrical networks $S_{11} = -S_{22}$. ^[19] For lossless reciprocal networks $|S_{11}| = |S_{22}|$ and $|S_{11}|^2 + |S_{12}|^2 = 1$. ^[20]

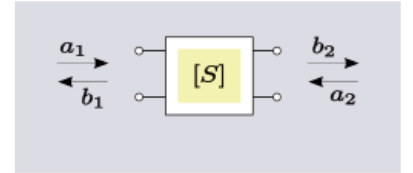


Fig. 17. Terminology of waves used in S -parameter definition.

Scattering transfer parameters (T-parameters)

Scattering transfer parameters, like scattering parameters, are defined in terms of incident and reflected waves. The difference is that T -parameters relate the waves at port 1 to the waves at port 2 whereas S -parameters relate the reflected waves to the incident waves. In this respect T -parameters fill the same role as $ABCD$ parameters and allow the T -parameters of cascaded networks to be calculated by matrix multiplication of the component networks. T -parameters, like $ABCD$ parameters, can also be called transmission parameters. The definition is, ^{[17][21]}

$$\begin{bmatrix} a_1 \\ b_1 \end{bmatrix} = \begin{bmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{bmatrix} \begin{bmatrix} b_2 \\ a_2 \end{bmatrix}$$

T -parameters are not as easy to measure directly as S -parameters. However, S -parameters are easily converted to T -parameters, see main article for details. ^[22]

Combinations of two-port networks

When two or more two-port networks are connected, the two-port parameters of the combined network can be found by performing matrix algebra on the matrices of parameters for the component two-ports. The matrix operation can be made particularly simple with an appropriate choice of two-port parameters to match the form of connection of the two-ports. For instance, the Z-parameters are best for series connected ports.

The combination rules need to be applied with care. Some connections (when dissimilar potentials are joined) result in the port condition being invalidated and the combination rule will no longer apply. A Brune test can be used to check the permissibility of the combination. This difficulty can be overcome by placing 1:1 ideal transformers on the outputs of the problem two-ports. This does not change the parameters of the two-ports, but does ensure that they will continue to meet the port condition when interconnected. An example of this problem is shown for series-series connections in figures 11 and 12 below.^[23]

Series-series connection

When two-ports are connected in a series-series configuration as shown in figure 10, the best choice of two-port parameter is the Z-parameters. The Z-parameters of the combined network are found by matrix addition of the two individual Z-parameter matrices.^{[24][25]}

$$[\mathbf{z}] = [\mathbf{z}]_1 + [\mathbf{z}]_2$$

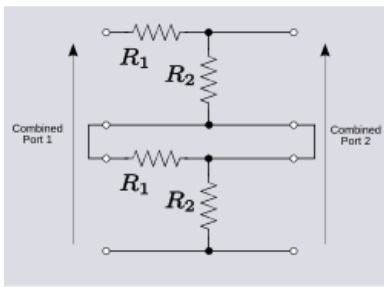


Fig. 11. Example of an improper connection of two-ports. R_1 of the lower two-port has been by-passed by a short circuit.

As mentioned above, there are some networks which will not yield directly to this analysis.^[23] A simple example is a two-port consisting of a L -network of resistors R_1 and R_2 . The Z-parameters for this network are;

$$[\mathbf{z}]_1 = \begin{bmatrix} R_1 + R_2 & R_2 \\ R_2 & R_2 \end{bmatrix}$$

Figure 11 shows two identical such networks connected in series-series. The total Z-parameters predicted by matrix addition are;

$$[\mathbf{z}] = [\mathbf{z}]_1 + [\mathbf{z}]_2 = 2[\mathbf{z}]_1 = \begin{bmatrix} 2R_1 + 2R_2 & 2R_2 \\ 2R_2 & 2R_2 \end{bmatrix}$$

However, direct analysis of the combined circuit shows that,

$$[\mathbf{z}] = \begin{bmatrix} R_1 + 2R_2 & 2R_2 \\ 2R_2 & 2R_2 \end{bmatrix}$$

The discrepancy is explained by observing that R_1 of the lower two-port has been by-passed by the short-circuit between two terminals of the output ports. This results in no current flowing through one terminal in each of the input ports of the two individual networks. Consequently, the port condition is broken for both the input ports of the original networks since current is still able to flow into the other terminal. This problem can be resolved by inserting an ideal transformer in the output port of at least one of the two-port networks. While this is a common text-book approach to presenting the theory of two-ports, the practicality of using transformers is a matter to be decided for each individual design.

Parallel-parallel connection

When two-ports are connected in a parallel-parallel configuration as shown in figure 13, the best choice of two-port parameter is the y-parameters. The y-parameters of the combined network are found by matrix addition of the two individual y-parameter matrices.^[26]

$$[\mathbf{y}] = [\mathbf{y}]_1 + [\mathbf{y}]_2$$

Series-parallel connection

When two-ports are connected in a series-parallel configuration as shown in figure 14, the best choice of two-port parameter is the h -parameters. The h -parameters of the combined network are found by matrix addition of the two individual h -parameter matrices.^[27]

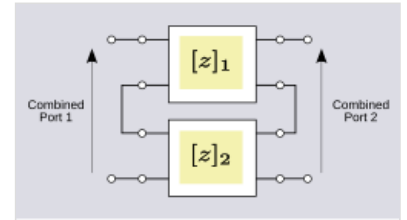


Fig. 10. Two two-port networks with input ports connected in series and output ports connected in series.

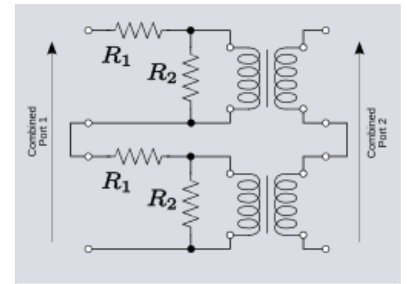


Fig. 12. Use of ideal transformers to restore the port condition to interconnected networks.

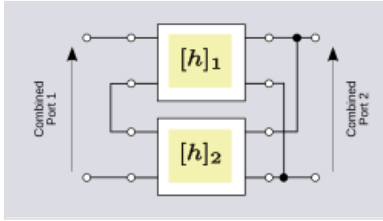


Fig. 14. Two two-port networks with input ports connected in series and output ports connected in parallel.

$$[\mathbf{h}] = [\mathbf{h}]_1 + [\mathbf{h}]_2$$

Parallel-series connection

When two-ports are connected in a parallel-series configuration as shown in figure 15, the best choice of two-port parameter is the g -parameters. The g -parameters of the combined network are found by matrix addition of the two individual g -parameter matrices.

$$[\mathbf{g}] = [\mathbf{g}]_1 + [\mathbf{g}]_2$$

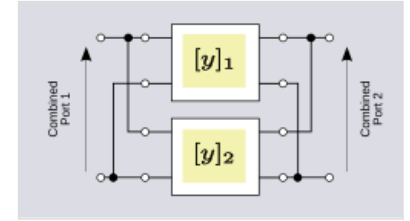


Fig. 13. Two two-port networks with input ports connected in parallel and output ports connected in parallel.

Cascade connection

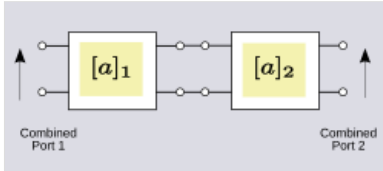


Fig. 16. Two two-port networks with the first's output port connected to the second's input port

When two-ports are connected with the output port of the first connected to the input port of the second (a cascade connection) as shown in figure 16, the best choice of two-port parameter is the $ABCD$ -parameters. The a -parameters of the combined network are found by matrix multiplication of the two individual a -parameter matrices.^[28]

$$[\mathbf{a}] = [\mathbf{a}]_1 \cdot [\mathbf{a}]_2$$

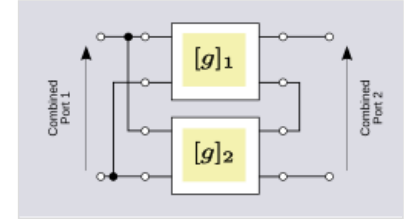


Fig. 15. Two two-port networks with input ports connected in parallel and output ports connected in series.

A chain of n two-ports may be combined by matrix multiplication of the n matrices. To combine a cascade of b -parameter matrices, they are again multiplied, but the multiplication must be carried out in reverse order, so that;

$$[\mathbf{b}] = [\mathbf{b}]_2 \cdot [\mathbf{b}]_1$$

Example

Suppose we have a two-port network consisting of a series resistor R followed by a shunt capacitor C . We can model the entire network as a cascade of two simpler networks:

$$[\mathbf{b}]_1 = \begin{bmatrix} 1 & -R \\ 0 & 1 \end{bmatrix}$$

$$[\mathbf{b}]_2 = \begin{bmatrix} 1 & 0 \\ -sC & 1 \end{bmatrix}$$

The transmission matrix for the entire network $[\mathbf{b}]$ is simply the matrix multiplication of the transmission matrices for the two network elements:

$$[\mathbf{b}] = [\mathbf{b}]_2 \cdot [\mathbf{b}]_1$$

$$= \begin{bmatrix} 1 & 0 \\ -sC & 1 \end{bmatrix} \begin{bmatrix} 1 & -R \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & -R \\ -sC & 1 + sCR \end{bmatrix}$$

Thus:

$$\begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = \begin{bmatrix} 1 & -R \\ -sC & 1 + sCR \end{bmatrix} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}$$

Interrelation of parameters

	[z]	[y]	[h]	[g]	[a]	[b]
[z]	$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$	$\frac{1}{\Delta[y]} \begin{bmatrix} y_{22} & -y_{12} \\ -y_{21} & y_{11} \end{bmatrix}$	$\frac{1}{h_{22}} \begin{bmatrix} \Delta[h] & h_{12} \\ -h_{21} & 1 \end{bmatrix}$	$\frac{1}{g_{11}} \begin{bmatrix} 1 & -g_{12} \\ g_{21} & \Delta[g] \end{bmatrix}$	$\frac{1}{a_{21}} \begin{bmatrix} a_{11} & \Delta[a] \\ 1 & a_{22} \end{bmatrix}$	$\frac{1}{b_{21}} \begin{bmatrix} -b_{22} & -1 \\ -\Delta[b] & -b_{11} \end{bmatrix}$
[y]	$\frac{1}{\Delta[z]} \begin{bmatrix} z_{22} & -z_{12} \\ -z_{21} & z_{11} \end{bmatrix}$	$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$	$\frac{1}{h_{11}} \begin{bmatrix} 1 & -h_{12} \\ h_{21} & \Delta[h] \end{bmatrix}$	$\frac{1}{g_{22}} \begin{bmatrix} \Delta[g] & g_{12} \\ -g_{21} & 1 \end{bmatrix}$	$\frac{1}{a_{12}} \begin{bmatrix} a_{22} & -\Delta[a] \\ -1 & a_{11} \end{bmatrix}$	$\frac{1}{b_{12}} \begin{bmatrix} -b_{11} & 1 \\ \Delta[b] & -b_{22} \end{bmatrix}$
[h]	$\frac{1}{z_{22}} \begin{bmatrix} \Delta[z] & z_{12} \\ -z_{21} & 1 \end{bmatrix}$	$\frac{1}{y_{11}} \begin{bmatrix} 1 & -y_{12} \\ y_{21} & \Delta[y] \end{bmatrix}$	$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$	$\frac{1}{\Delta[g]} \begin{bmatrix} g_{22} & -g_{12} \\ -g_{21} & g_{11} \end{bmatrix}$	$\frac{1}{a_{22}} \begin{bmatrix} a_{12} & \Delta[a] \\ -1 & a_{21} \end{bmatrix}$	$\frac{1}{b_{11}} \begin{bmatrix} -b_{12} & 1 \\ -\Delta[b] & -b_{21} \end{bmatrix}$
[g]	$\frac{1}{z_{11}} \begin{bmatrix} 1 & -z_{12} \\ z_{21} & \Delta[z] \end{bmatrix}$	$\frac{1}{y_{22}} \begin{bmatrix} \Delta[y] & y_{12} \\ -y_{21} & 1 \end{bmatrix}$	$\frac{1}{\Delta[h]} \begin{bmatrix} h_{22} & -h_{12} \\ -h_{21} & h_{11} \end{bmatrix}$	$\begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix}$	$\frac{1}{a_{11}} \begin{bmatrix} a_{21} & -\Delta[a] \\ 1 & a_{12} \end{bmatrix}$	$\frac{1}{b_{22}} \begin{bmatrix} -b_{21} & -1 \\ \Delta[b] & -b_{12} \end{bmatrix}$
[a]	$\frac{1}{z_{21}} \begin{bmatrix} z_{11} & \Delta[z] \\ 1 & z_{22} \end{bmatrix}$	$\frac{1}{y_{21}} \begin{bmatrix} -y_{22} & -1 \\ -\Delta[y] & -y_{11} \end{bmatrix}$	$\frac{1}{h_{21}} \begin{bmatrix} -\Delta[h] & -h_{11} \\ -h_{22} & -1 \end{bmatrix}$	$\frac{1}{g_{21}} \begin{bmatrix} 1 & g_{22} \\ g_{11} & \Delta[g] \end{bmatrix}$	$\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix}$	$\frac{1}{\Delta[b]} \begin{bmatrix} b_{22} & -b_{12} \\ -b_{21} & b_{11} \end{bmatrix}$
[b]	$\frac{1}{z_{12}} \begin{bmatrix} z_{22} & -\Delta[z] \\ -1 & z_{11} \end{bmatrix}$	$\frac{1}{y_{12}} \begin{bmatrix} -y_{11} & 1 \\ \Delta[y] & -y_{22} \end{bmatrix}$	$\frac{1}{h_{12}} \begin{bmatrix} 1 & -h_{11} \\ -h_{22} & \Delta[h] \end{bmatrix}$	$\frac{1}{g_{12}} \begin{bmatrix} -\Delta[g] & g_{22} \\ g_{11} & -1 \end{bmatrix}$	$\frac{1}{\Delta[a]} \begin{bmatrix} a_{22} & -a_{12} \\ -a_{21} & a_{11} \end{bmatrix}$	$\begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix}$

Where $\Delta[\mathbf{x}]$ is the determinant of $[\mathbf{x}]$.

Certain pairs of matrices have a particularly simple relationship. The admittance parameters are the matrix inverse of the impedance parameters, the inverse hybrid parameters are the matrix inverse of the hybrid parameters, and the $[\mathbf{b}]$ form of the *ABCD*-parameters is the matrix inverse of the $[\mathbf{a}]$ form. That is,

$$\begin{aligned} [\mathbf{y}] &= [\mathbf{z}]^{-1} \\ [\mathbf{g}] &= [\mathbf{h}]^{-1} \\ [\mathbf{b}] &= [\mathbf{a}]^{-1} \end{aligned}$$

Networks with more than two ports

While two port networks are very common (e.g., amplifiers and filters), other electrical networks such as directional couplers and circulators have more than 2 ports. The following representations are also applicable to networks with an arbitrary number of ports:

- Admittance (*y*) parameters
- Impedance (*z*) parameters
- Scattering (*S*) parameters

For example, three-port impedance parameters result in the following relationship:

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & Z_{13} \\ Z_{21} & Z_{22} & Z_{23} \\ Z_{31} & Z_{32} & Z_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

However the following representations are necessarily limited to two-port devices:

- Hybrid (*h*) parameters
- Inverse hybrid (*g*) parameters
- Transmission (*ABCD*) parameters
- Scattering transfer (*T*) parameters

Collapsing a two-port to a one port

A two-port network has four variables with two of them being independent. If one of the ports is terminated by a load with no independent sources, then the load enforces a relationship between the voltage and current of that port. A degree of freedom is lost. The circuit now has only one independent parameter. The two-port becomes a one-port impedance to the remaining independent variable.

For example, consider impedance parameters

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Connecting a load, Z_L onto port 2 effectively adds the constraint

$$V_2 = -Z_L I_2$$

The negative sign is because the positive direction for I_2 is directed into the two-port instead of into the load. The augmented equations become

$$\begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} I_2 \\ -Z_L I_2 &= Z_{21} I_1 + Z_{22} I_2 \end{aligned}$$

The second equation can be easily solved for I_2 as a function of I_1 and that expression can replace I_2 in the first equation leaving V_1 (and V_2 and I_2) as functions of I_1

$$\begin{aligned} I_2 &= -\frac{Z_{21}}{Z_L + Z_{22}} I_1 \\ V_1 &= Z_{11} I_1 - \frac{Z_{12} Z_{21}}{Z_L + Z_{22}} I_1 \\ &= \left(Z_{11} - \frac{Z_{12} Z_{21}}{Z_L + Z_{22}} \right) I_1 = Z_{in} I_1 \end{aligned}$$

So, in effect, I_1 sees an input impedance Z_{in} and the two-port's effect on the input circuit has been effectively collapsed down to a one-port; i.e., a simple two terminal impedance.

See also

- [Admittance parameters](#)
- [Impedance parameters](#)
- [Scattering parameters](#)
- [Transfer-matrix method \(optics\)](#) for reflection/transmission calculation of light waves in transparent layers
- [Ray transfer matrix](#) for calculation of paraxial propagation of a light ray

Notes

1. The emitter-leg resistors counteract any current increase by decreasing the transistor V_{BE} . That is, the resistors R_E cause negative feedback that opposes change in current. In particular, any change in output voltage results in less change in current than without this feedback, which means the output resistance of the mirror has increased.
2. The double vertical bar denotes a [parallel](#) connection of the resistors: $R_1 \parallel R_2 = 1/(1/R_1 + 1/R_2)$.

References

1. Gray, §3.2, p. 172
2. Jaeger, §10.5 §13.5 §13.8
3. Jasper J. Goedbloed. "Reciprocity and EMC measurements" (<http://www.emcs.org/acstrial/newsletters/summer03/jasper.pdf>) (PDF). EMCS. Retrieved 28 April 2014.
4. Nahvi, p. 311.
5. Matthaei et al, pp. 70–72.
6. Matthaei et al, p. 27.
7. Matthaei et al, p. 29.
8. 56 IRE 28.S2, p. 1543
9. AIEE-IRE committee report, p. 725
10. IEEE Std 218-1956
11. Matthaei et al, p. 26.
12. Ghosh, p. 353.
13. A. Chakrabarti, p. 581, ISBN 81-7700-000-4, Dhanpat Rai & Co pvt. ltd.
14. Farago, p. 102.
15. Clayton, p. 271.
16. Sinha, Rakesh (December 2022). "Computer-Aided Design of Multisection Matching Networks With Desired Phase-Shift" (<https://ieeexplore.ieee.org/document/9865126/>). *IEEE Transactions on Circuits and Systems II: Express Briefs*. **69** (12): 5074–5078. doi:10.1109/TCSII.2022.3201114 (<https://doi.org/10.1109/9%2FTCSII.2022.3201114>). ISSN 1558-3791 (<https://search.worldcat.org/issn/1558-3791>).
17. Vasileska & Goodnick, p. 137
18. Egan, pp. 11–12
19. Carlin, p. 304
20. Matthaei et al, p. 44.
21. Egan, pp. 12–15
22. Egan, pp. 13–14
23. Farago, pp. 122–127.
24. Ghosh, p. 371.
25. Farago, p. 128.
26. Ghosh, p. 372.
27. Ghosh, p. 373.
28. Farago, pp. 128–134.

Bibliography

- Carlin, HJ, Civalleri, PP, *Wideband circuit design*, CRC Press, 1998. ISBN 0-8493-7897-4.
- William F. Egan, *Practical RF system design*, Wiley-IEEE, 2003 ISBN 0-471-20023-9.
- Farago, PS, *An Introduction to Linear Network Analysis*, The English Universities Press Ltd, 1961.
- Gray, P.R.; Hurst, P.J.; Lewis, S.H.; Meyer, R.G. (2001). *Analysis and Design of Analog Integrated Circuits* (4th ed.). New York: Wiley. ISBN 0-471-32168-0.
- Ghosh, Smarajit, *Network Theory: Analysis and Synthesis*, Prentice Hall of India ISBN 81-203-2638-5.
- Jaeger, R.C.; Blalock, T.N. (2006). *Microelectronic Circuit Design* (3rd ed.). Boston: McGraw-Hill. ISBN 978-0-07-319163-8.
- Matthaei, Young, Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, McGraw-Hill, 1964.
- Mahmood Nahvi, Joseph Edminister, *Schaum's outline of theory and problems of electric circuits*, McGraw-Hill Professional, 2002 ISBN 0-07-139307-2.
- Dragica Vasileska, Stephen Marshall Goodnick, *Computational electronics*, Morgan & Claypool Publishers, 2006 ISBN 1-59829-056-8.
- Clayton R. Paul, *Analysis of Multiconductor Transmission Lines*, John Wiley & Sons, 2008 ISBN 0470131543, 9780470131541.

h-parameters history

- D. A. Alsberg, "Transistor metrology", *IRE Convention Record*, part 9, pp. 39–44, 1953.
 - also published as "Transistor metrology" (<https://ieeexplore.ieee.org/document/1471877/>), *Transactions of the IRE Professional Group on Electron Devices*, vol. ED-1, iss. 3, pp. 12–17, August 1954.
- AIEE-IRE joint committee, "Proposed methods of testing transistors" (<https://ieeexplore.ieee.org/stamp/stamp.jsp?arnumber=6372229>), *Transactions of the American Institute of Electrical Engineers: Communications and Electronics*, pp. 725–740, January 1955.
- "IRE Standards on solid-state devices: methods of testing transistors, 1956" (<https://ieeexplore.ieee.org/document/4051913/>), *Proceedings of the IRE*, vol. 44, iss. 11, pp. 1542–1561, November, 1956.
- *IEEE Standard Methods of Testing Transistors* (<https://ieeexplore.ieee.org/document/7370855/>), IEEE Std 218-1956.

Retrieved from "https://en.wikipedia.org/w/index.php?title=Two-port_network&oldid=1308927575"